

---

# **DIGITAL SYSTEM DESIGN APPLICATIONS**

---

## **Experiment 2**

### **MSI Components**

**Berfin Duman**  
040190108

## Contents

<b>1</b>	<b>DECODER</b>	<b>3</b>
1.1	Truth Table of 4x16 Decoder . . . . .	3
1.2	Verilog Code, Testbench Code and Behavioral Simulation . . . . .	3
1.3	RTL and Technology Schematics . . . . .	6
1.4	Implementation Parts and Reports . . . . .	9
<b>2</b>	<b>Priority Encoder</b>	<b>10</b>
2.1	Truth Table of 4 to 2 Priority Encoder . . . . .	10
2.2	Logic Statements of Outputs . . . . .	11
2.3	Logic Diagram . . . . .	12
2.4	Verilog Code, Testbench Code and Behavioral Simulation . . . . .	12
2.5	Rtl and Technology Schematics . . . . .	14
2.6	Implementation Parts and Reports . . . . .	16
2.7	Behavioral Priority Encoder . . . . .	16
2.8	Implementation Parts and Comparison Reports . . . . .	17
<b>3</b>	<b>MULTIPLEXER</b>	<b>18</b>
3.1	Verilog Code, Testbench Code and Behavioral Simulation . . . . .	18
3.2	Rtl and Technology Schematic . . . . .	20
3.3	Implementation Parts and Reports . . . . .	23
3.4	Behavioral MULTIPLEXER . . . . .	23
3.5	Implementation Parts and Comparison Reports . . . . .	24
<b>4</b>	<b>DEMUX</b>	<b>24</b>
4.1	Verilog Code, Testbench Code and Behavioral Simulation . . . . .	24
4.2	Rtl and Technology Schematic . . . . .	27
4.3	Implementation Parts and Reports . . . . .	29

# 1 DECODER

First of all, i prepared a new folder which called "week2" for experiment2. I opened new rtl project called project\_1 on experiment2 folder. I created MSILibrary.v as sources and added constrain file which I downloaded from ninova .Then I added true fpga board, as we were asked to do so in the report. And as expected from the assignment, I started writing Decoder verilog code.

## 1.1 Truth Table of 4x16 Decoder

I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	O <sub>15</sub>	O <sub>14</sub>	O <sub>13</sub>	O <sub>12</sub>	O <sub>11</sub>	O <sub>10</sub>	O <sub>9</sub>	O <sub>8</sub>	O <sub>7</sub>	O <sub>6</sub>	O <sub>5</sub>	O <sub>4</sub>	O <sub>3</sub>	O <sub>2</sub>	O <sub>1</sub>	O <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

Table 1: Decoder Truth Table

## 1.2 Verilog Code, Testbanch Code and Behavioral Simulation

I wrote DECODER module in MSILibrary. This module have 4- bit inputs wihchcalled IN, and 16- bit output, which called OUT. I wrote this module usin always and case structure as stated in the report. Therefore I did behovioral modelling in module. (Decoder verilog code is available in Listing 1)

And then i created new design source called top\_module.v. The same way, I added 8-bit sw, and 4-bit btns as inputs and 8-bit led, 7-bit cat, 4-bit an and finally 1-bit dp as output on the top\_module module. (I used the same top\_module in the following stages and imported all the desired MSI Components by connecting them to the inputs and outputs as desired. At the relevant stage, I removed the module I was interested in from the comment line and expressed the others as comment lines.) And I instantianed the DECODER module with the name decoder1 in the top module. I connected decoder1 module inputs and outputs to sw,dp,cat and led. Then i connected an output logic 0 and 1as expected. (Top\_module verilog ,which i used all stages, is code available in Listing2 )

Listing 1: Decoder Verilog Code: Sysyem\_Lib.v

```

1  `timescale 1ns / 1ps
2  module DECODER(
3      input  [3:0] IN,
4      output reg [15:0] OUT
5  );
6      always @(IN)
7      begin
8          case (IN)
9              4'b0000: OUT = 16'b0000000000000001;
10             4'b0001: OUT = 16'b0000000000000010;
11             4'b0010: OUT = 16'b0000000000000100;
12             4'b0011: OUT = 16'b00000000000001000;
13             4'b0100: OUT = 16'b00000000000010000;
14             4'b0101: OUT = 16'b00000000000100000;
15             4'b0110: OUT = 16'b00000000001000000;
16             4'b0111: OUT = 16'b00000000010000000;
17             4'b1000: OUT = 16'b00000000100000000;
18             4'b1001: OUT = 16'b00000001000000000;
19             4'b1010: OUT = 16'b00000010000000000;
20             4'b1011: OUT = 16'b00000100000000000;
21             4'b1100: OUT = 16'b00001000000000000;
22             4'b1101: OUT = 16'b00010000000000000;
23             4'b1110: OUT = 16'b00100000000000000;
24             4'b1111: OUT = 16'b10000000000000000;
25             default: OUT = 16'b00000000000000000;
26         endcase
27     end
28 endmodule

```

Listing 2: Top\_Module Verilog Code

```

1      input  [3:0] btn,
2      output [7:0] led,
3      output [6:0] cat,
4      output [3:0] an,
5      output dp);
6
7      //DEMULTIPLEXER demux1(.D(sw[0]),.S(btn[1:0]),
8          .O(led[3:0]));
9      //MULTIPLEXER mux1(.D(sw[3:0]),.S(btn[1:0]),.O(led[0]));
10     //ENCODER encoder1(.IN(sw[3:0]),.OUT(led[1:0]),.V(led[7]));
11     DECODER decoder1(.IN(sw[3:0]),.OUT({dp,cat,led}));
12     assign an = 4'b1110;
13 endmodule

```

For the simulation, i wrote the testbench, i paid attention to show all cases in testbench code.(For testbench code, the controllers and wires and their top\_module connections are the same at all stages, only the test parts are different.) And i made behavioral simulation. (Test bench verilog code is available in L2 and behavioral simulation image is available in Fig1)

Listing 3: Decoder TestBench Verilog Code

```
1  reg [3:0] BTN;
2  wire [7:0] LED;
3  wire [6:0] CAT;
4  wire [3:0] AN;
5  wire DP;
6  top_module uut(.sw(SW),.btn(BTN),
7  .led(LED),.cat(CAT),.an(AN),.dp(DP));
8  initial
9      begin
10         SW=4'b0000;
11         #10 SW=4'b0001;
12         #10 SW=4'b0010;
13         #10 SW=4'b0011;
14         #10 SW=4'b0100;
15         #10 SW=4'b0101;
16         #10 SW=4'b0110;
17         #10 SW=4'b0111;
18         #10 SW=4'b1000;
19         #10 SW=4'b1001;
20         #10 SW=4'b1010;
21         #10 SW=4'b1011;
22         #10 SW=4'b1100;
23         #10 SW=4'b1101;
24         #10 SW=4'b1110;
25         #10 SW=4'b1111;
26         #10
27         $finish;
28     end
endmodule
```

 


Figure 1: Decoder Behavioral Simulation

### 1.3 RTL and Technology Schematics

For the synthesise and more i added the master constraint file in properly, so i uncomment some leds, switch, buttons and seven-segment display ,and I connected ports as with correct top\_module input and output names.(Organized constrain file is available in F2 )

```
##Switches
set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 } [get_ports { sw[0] }]; #IO_L24N_T3_R30_15 Sch=sw[0]
set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 } [get_ports { sw[1] }]; #IO_L3N_T0_D08_EM0CLK_14 Sch=sw[1]
set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 } [get_ports { sw[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 } [get_ports { sw[3] }]; #IO_L13N_T2_MR0C_14 Sch=sw[3]
set_property -dict { PACKAGE_PIN R17      IOSTANDARD LVCMOS33 } [get_ports { sw[4] }]; #IO_L12N_T1_MR0C_14 Sch=sw[4]
set_property -dict { PACKAGE_PIN T18      IOSTANDARD LVCMOS33 } [get_ports { sw[5] }]; #IO_L7N_T1_D10_14 Sch=sw[5]
set_property -dict { PACKAGE_PIN U18      IOSTANDARD LVCMOS33 } [get_ports { sw[6] }]; #IO_L17N_T2_A13_D29_14 Sch=sw[6]
set_property -dict { PACKAGE_PIN R13      IOSTANDARD LVCMOS33 } [get_ports { sw[7] }]; #IO_L5N_T0_D07_14 Sch=sw[7]

## LEDs
set_property -dict { PACKAGE_PIN H17      IOSTANDARD LVCMOS33 } [get_ports { led[0] }]; #IO_L18P_T2_A24_15 Sch=led[0]
set_property -dict { PACKAGE_PIN K15      IOSTANDARD LVCMOS33 } [get_ports { led[1] }]; #IO_L24P_T3_R31_15 Sch=led[1]
set_property -dict { PACKAGE_PIN J13      IOSTANDARD LVCMOS33 } [get_ports { led[2] }]; #IO_L17N_T2_A25_15 Sch=led[2]
set_property -dict { PACKAGE_PIN N14      IOSTANDARD LVCMOS33 } [get_ports { led[3] }]; #IO_L8P_T1_D11_14 Sch=led[3]
set_property -dict { PACKAGE_PIN R18      IOSTANDARD LVCMOS33 } [get_ports { led[4] }]; #IO_L7P_T1_D09_14 Sch=led[4]
set_property -dict { PACKAGE_PIN V17      IOSTANDARD LVCMOS33 } [get_ports { led[5] }]; #IO_L18N_T2_A11_D27_14 Sch=led[5]
set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 } [get_ports { led[6] }]; #IO_L17P_T2_A14_D30_14 Sch=led[6]
set_property -dict { PACKAGE_PIN U16      IOSTANDARD LVCMOS33 } [get_ports { led[7] }]; #IO_L18P_T2_A12_D28_14 Sch=led[7]

##7 segment display
set_property -dict { PACKAGE_PIN T10      IOSTANDARD LVCMOS33 } [get_ports { cat[0] }]; #IO_L24N_T3_A00_D16_14 Sch=ca
set_property -dict { PACKAGE_PIN R10      IOSTANDARD LVCMOS33 } [get_ports { cat[1] }]; #IO_25_14 Sch=cb
set_property -dict { PACKAGE_PIN K16      IOSTANDARD LVCMOS33 } [get_ports { cat[2] }]; #IO_25_15 Sch=cc
set_property -dict { PACKAGE_PIN K13      IOSTANDARD LVCMOS33 } [get_ports { cat[3] }]; #IO_L17P_T2_A26_15 Sch=cd
set_property -dict { PACKAGE_PIN P15      IOSTANDARD LVCMOS33 } [get_ports { cat[4] }]; #IO_L13P_T2_MR0C_14 Sch=ce
set_property -dict { PACKAGE_PIN T11      IOSTANDARD LVCMOS33 } [get_ports { cat[5] }]; #IO_L19P_T3_A10_D26_14 Sch=cf
set_property -dict { PACKAGE_PIN L18      IOSTANDARD LVCMOS33 } [get_ports { cat[6] }]; #IO_L4P_T0_D04_14 Sch=cg
set_property -dict { PACKAGE_PIN H15      IOSTANDARD LVCMOS33 } [get_ports { dp }]; #IO_L19N_T3_A21_VREF_15 Sch=dp
set_property -dict { PACKAGE_PIN U17      IOSTANDARD LVCMOS33 } [get_ports { an[0] }]; #IO_L23P_T3_F0E_B_15 Sch=an[0]
set_property -dict { PACKAGE_PIN R18      IOSTANDARD LVCMOS33 } [get_ports { an[1] }]; #IO_L23N_T3_FWE_B_15 Sch=an[1]
set_property -dict { PACKAGE_PIN T9       IOSTANDARD LVCMOS33 } [get_ports { an[2] }]; #IO_L24P_T3_A01_D17_14 Sch=an[2]
set_property -dict { PACKAGE_PIN J14      IOSTANDARD LVCMOS33 } [get_ports { an[3] }]; #IO_L19P_T3_A22_15 Sch=an[3]
set_property -dict { PACKAGE_PIN P14      IOSTANDARD LVCMOS33 } [get_ports { an[4] }]; #IO_L6N_T1_D12_14 Sch=an[4]
set_property -dict { PACKAGE_PIN T14      IOSTANDARD LVCMOS33 } [get_ports { an[5] }]; #IO_L14P_T2_SR0C_14 Sch=an[5]
set_property -dict { PACKAGE_PIN K2       IOSTANDARD LVCMOS33 } [get_ports { an[6] }]; #IO_L23P_T3_35 Sch=an[6]
set_property -dict { PACKAGE_PIN U13      IOSTANDARD LVCMOS33 } [get_ports { an[7] }]; #IO_L23N_T3_A02_D18_14 Sch=an[7]

##Buttons
set_property -dict { PACKAGE_PIN N17      IOSTANDARD LVCMOS33 } [get_ports { btn[0] }]; #IO_L9P_T1_D08_14 Sch=btn0
set_property -dict { PACKAGE_PIN M18      IOSTANDARD LVCMOS33 } [get_ports { btn[1] }]; #IO_L4N_T0_D05_14 Sch=btn1
set_property -dict { PACKAGE_PIN P17      IOSTANDARD LVCMOS33 } [get_ports { btn[2] }]; #IO_L12P_T1_MR0C_14 Sch=btn2
set_property -dict { PACKAGE_PIN M17      IOSTANDARD LVCMOS33 } [get_ports { btn[3] }]; #IO_L10N_T1_D15_14 Sch=btn3

##Set Timing Constrains
set_max_delay 10 -from [all_inputs] -to [all_outputs]
```

Figure 2: Organized Constrains File

Then, I obtained Rtl and technology schematics by performing Rtl analysis and synthesis, respectively.

It refers to the RTL-ROM (Read-Only Memory) design that we see in the RTL schematic.

RTL ROM is used to provide certain fixed data based on the outputs of the design in the case, as we mentioned in the decoder module.

There are 16 truth tables in total in the technology schematic, and since they have 4 entries, they appear as LUT4 tables. And when we look at the truth table of these tables, we see 16 combinations and outputs related to 4 inputs. In its output, I observed that the combination corresponding to whichever output it was connected to was 1 and the others were 0. That is, each LUT represents a specific output and implements logic expressions related to the input signals.

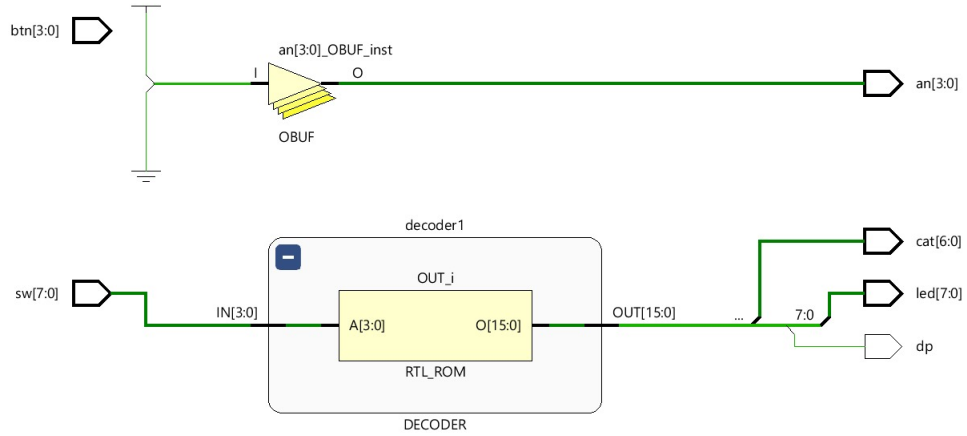


Figure 3: Decoder RTL Schematic

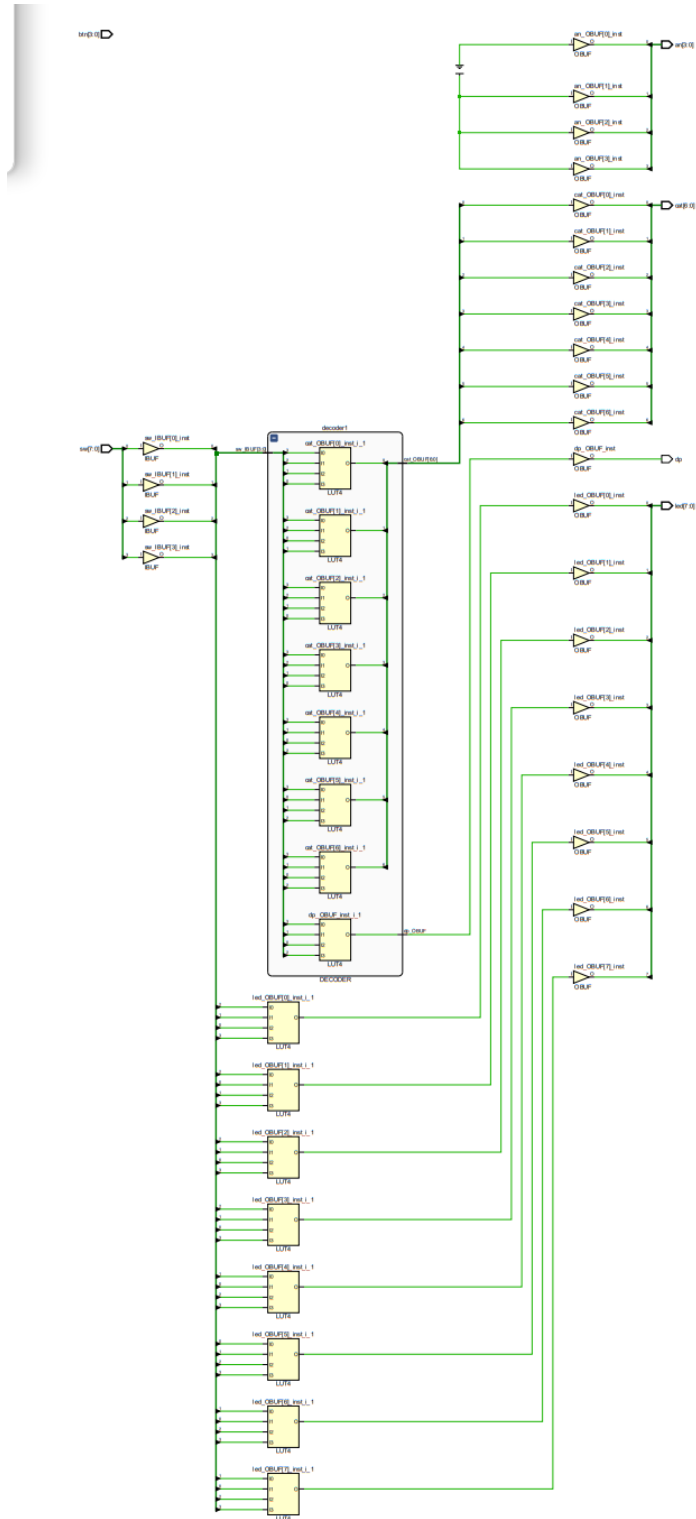


Figure 4: Decoder Technology Schematic



## 1.4 Implementation Parts and Reports

Then, I moved on to the implementation phase and examined the timing reports of the implementation results. As can be seen (Fig5), the max delay is 10,530 from s3 to cat4, and the following 3 ports appear to have a delay above +10. To accommodate this, I added a timing constraint to the design, as requested in the report, that would ensure that the circuit's largest pad-to-pad delay was 10ns. I did this by uncommenting the code in the last line of the constrain file.

```
###Set Timing Constrain
set_max_delay 10 -from [all_inputs] -to [all_outputs]
```

And when I came to the implementation step again, I saw that the timing summary had changed and the max\_delay had been reduced from sw0 to led7 to 9.774, as I wanted (Fig6). This restriction code I added enabled the design to optimize the delay and keep it at 10ns max.

Combinational Delays						
From Port	To Port	Max Delay	Max Process Corner	Min Process Corner	Min Delay	
sw[3]	cat[4]	10.530	SLOW	FAST		3.381
sw[0]	cat[1]	10.277	SLOW	FAST		3.269
sw[0]	cat[0]	10.075	SLOW	FAST		3.220
sw[3]	led[2]	10.046	SLOW	FAST		3.170
sw[3]	led[0]	9.968	SLOW	FAST		3.124
sw[3]	dp	9.947	SLOW	FAST		3.125
sw[3]	led[4]	9.920	SLOW	FAST		3.149
sw[3]	cat[3]	9.914	SLOW	FAST		3.148
sw[0]	led[7]	9.878	SLOW	FAST		3.098
sw[0]	led[6]	9.826	SLOW	FAST		3.080
sw[0]	cat[5]	9.784	SLOW	FAST		3.069
sw[1]	cat[1]	9.693	SLOW	FAST		3.063
sw[0]	led[5]	9.620	SLOW	FAST		3.019
sw[1]	cat[4]	9.498	SLOW	FAST		2.950
sw[3]	led[1]	9.498	SLOW	FAST		2.954
sw[1]	cat[0]	9.493	SLOW	FAST		3.011
sw[2]	led[2]	9.452	SLOW	FAST		2.936
sw[2]	cat[4]	9.412	SLOW	FAST		2.970
sw[0]	cat[4]	9.402	SLOW	FAST		2.897
sw[2]	led[0]	9.376	SLOW	FAST		2.885
sw[3]	led[7]	9.365	SLOW	FAST		2.909
sw[2]	led[4]	9.326	SLOW	FAST		2.909
sw[3]	cat[1]	9.286	SLOW	FAST		2.814
sw[3]	cat[5]	9.280	SLOW	FAST		2.946
sw[2]	cat[5]	9.258	SLOW	FAST		2.858
sw[1]	led[6]	9.239	SLOW	FAST		2.872
sw[2]	cat[1]	9.213	SLOW	FAST		2.903

Figure 5: Decoder Timing Summary No Forcing For Max Delay

Tcl Console

Messages

Log

Reports

Design Runs

Power

DRC

Timing

x

Q

⌵

⌶

⌵

⌶

⌵

⌶

⌵

Q

Combinational Delays

General Information

Timer Settings

Design Timing Summary

> Check Timing (12)

Intra-Clock Paths

Inter-Clock Paths

> Other Path Groups

User Ignored Paths

> Unconstrained Paths

▼ Datasheet

Input Ports Setup/Hold

Output Ports Clock-to-out

Combinational Delays

Setup between Clocks

From Port

To Port

Max Delay

1

Max Process Corner

sw[0]

led[7]

9.774

SLOW

sw[0]

cat[0]

9.744

SLOW

sw[3]

led[0]

9.579

SLOW

sw[0]

cat[1]

9.501

SLOW

sw[0]

cat[5]

9.474

SLOW

sw[2]

cat[1]

9.401

SLOW

sw[3]

dp

9.390

SLOW

sw[3]

led[2]

9.356

SLOW

sw[3]

cat[4]

9.351

SLOW

sw[0]

led[2]

9.342

SLOW

sw[1]

led[0]

9.327

SLOW

sw[0]

cat[6]

9.321

SLOW

sw[1]

cat[0]

9.236

SLOW

sw[0]

led[3]

9.218

SLOW

sw[3]

led[6]

9.207

SLOW

sw[1]

cat[1]

9.203

SLOW

sw[0]

led[6]

9.197

SLOW

sw[3]

cat[3]

9.153

SLOW

sw[2]

cat[0]

9.150

SLOW

sw[1]

led[2]

9.114

SLOW

sw[1]

cat[5]

9.087

SLOW

sw[0]

led[0]

9.084

SLOW

sw[2]

led[7]

9.070

SLOW

Figure 6: Decoder Timing Summary Forcing For Max Delay

Then, I made the module testable on FPGA by creating a bitstream.

## 2 Priority Encoder

### 2.1 Truth Table of 4 to 2 Priority Encoder

I <sub>3</sub>	I <sub>2</sub>	I <sub>1</sub>	I <sub>0</sub>	O <sub>1</sub>	O <sub>0</sub>	V
0	0	0	0	x	x	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

Table 2: Decoder Truth Table

## 2.2 Logic Statements of Outputs

$O1 =$

		$I_2 I_3$			
$I_0 I_1$		00	01	11	10
00		X	1	1	1
01			1	1	1
11	$I_0$		1	1	1
10			1	1	1

Handwritten annotations: A blue bracket under the last two columns is labeled  $I_3$ . A green bracket to the right of the last two columns is labeled  $I_1$ . A red bracket above the last two columns is labeled  $I_2$ . An orange bracket to the left of the last two rows is labeled  $I_0$ .

Figure 7:  $O1 = I2 + I3$  Statement

$O0 =$

		$I_2 I_3$			
$I_0 I_1$		00	01	11	10
00		X	1	1	
01		1	1	1	
11	$I_0$	1	1	1	
10			1	1	

Handwritten annotations: A blue bracket under the last two columns is labeled  $I_3$ . A green bracket to the right of the last two columns is labeled  $I_1$ . A red bracket above the last two columns is labeled  $I_2$ . An orange bracket to the left of the last two rows is labeled  $I_0$ .

Figure 8:  $O0 = I3 + I1(I2)'$  Statement

$V_2$

		$I_2 I_3$			
$I_0 I_1$		00	01	11	10
00			1	1	1
01		1	1	1	1
11	$I_0$	1	1	1	1
10		1	1	1	1

Handwritten annotations: A blue bracket under the last two columns is labeled  $I_3$ . A green bracket to the right of the last two columns is labeled  $I_1$ . A red bracket above the last two columns is labeled  $I_2$ . An orange bracket to the left of the last two rows is labeled  $I_0$ .

Figure 9:  $V = I0 + I1 + I2 + I3$  Statement

## 2.3 Logic Diagram

 


Figure 10: Logic Diagram of the Reduced Statements

## 2.4 Verilog Code, Testbench Code and Behavioral Simulation

I wrote the verilog code for the encoder module to have 4-bit input, 2-bit output and 1 V output. In order for the module to exhibit priority encoder behavior, I created a structural code using the reduced statments, which I obtained with the Karnaugh map, on the primitive gates provided by Verilog. (L4).

Listing 4: Priority Encoder with Primitive Gates Verilog Code

```

1 output [1:0] OUT,
2 output V );
3 wire temp1;
4 wire temp2;
5 wire temp3;
6 or or_module(OUT[1],IN[3], IN[2]);
7 not not_module(temp1, IN[2] );
8 and and_module (temp2, temp1, IN[1]);
9 or or_module2(OUT[0], IN[3], temp2);
10 or or_module3 (temp3, IN[0], IN[1]);
11 or or_module4 (V, OUT[1], temp3);
12 endmodule

```

In the top\_module I created, I commented the Decoder module then instantiated the Encoder as encoder1. For this, I connected the appropriate inputs and outputs to the encoder1 module as requested: I connected the least significant 4 bits of sw as IN, the least significant two bits of led as Output, and the most significant bit of led as V. (L5)

Listing 5: Top\_Module PE Verilog Code

```

13 input [3:0] btn,
14 output [7:0] led,
15 output [6:0] cat,
16 output [3:0] an,
17 output dp);
18 ENCODER encoder1(.IN(sw[3:0]),.OUT(led[1:0]),.V(led[7]));

```

```

19     assign an = 4'b1110;
20 endmodule

```

Listing 6: Testbench PE Verilog Code

```

29     reg [3:0] BTN;
30     wire [7:0] LED;
31     wire [6:0] CAT;
32     wire [3:0] AN;
33     wire DP;
34     top_module uut(.sw(SW),.btn(BTN),
35                   .led(LED),.cat(CAT),.an(AN),.dp(DP));
36     initial
37     begin
38         SW=4'b0000;
39         #10 SW=4'b0001;
40         #10 SW=4'b001x;
41         #10 SW=4'b01xx;
42         #10 SW=4'b1xxx;
43         #10
44         $finish;
45     end
endmodule

```

I performed testbench in both structural and behavioral codes. (Fig11, Fig12) We can also observe the output, as it is stated in the module that the 00 status of the input is not given in the structural one, while in the behavioral case, XX output is given at 00 input.



Figure 11: Structural P Encoder Behavioral Simulation

 


Figure 12: Behavioral P Encoder Behavioral Simulation

## 2.5 Rtl and Technology Schematics

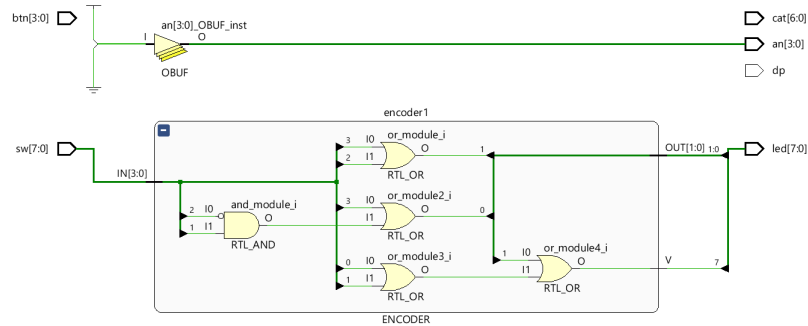


Figure 13: Priority Encoder Rtl Schematic

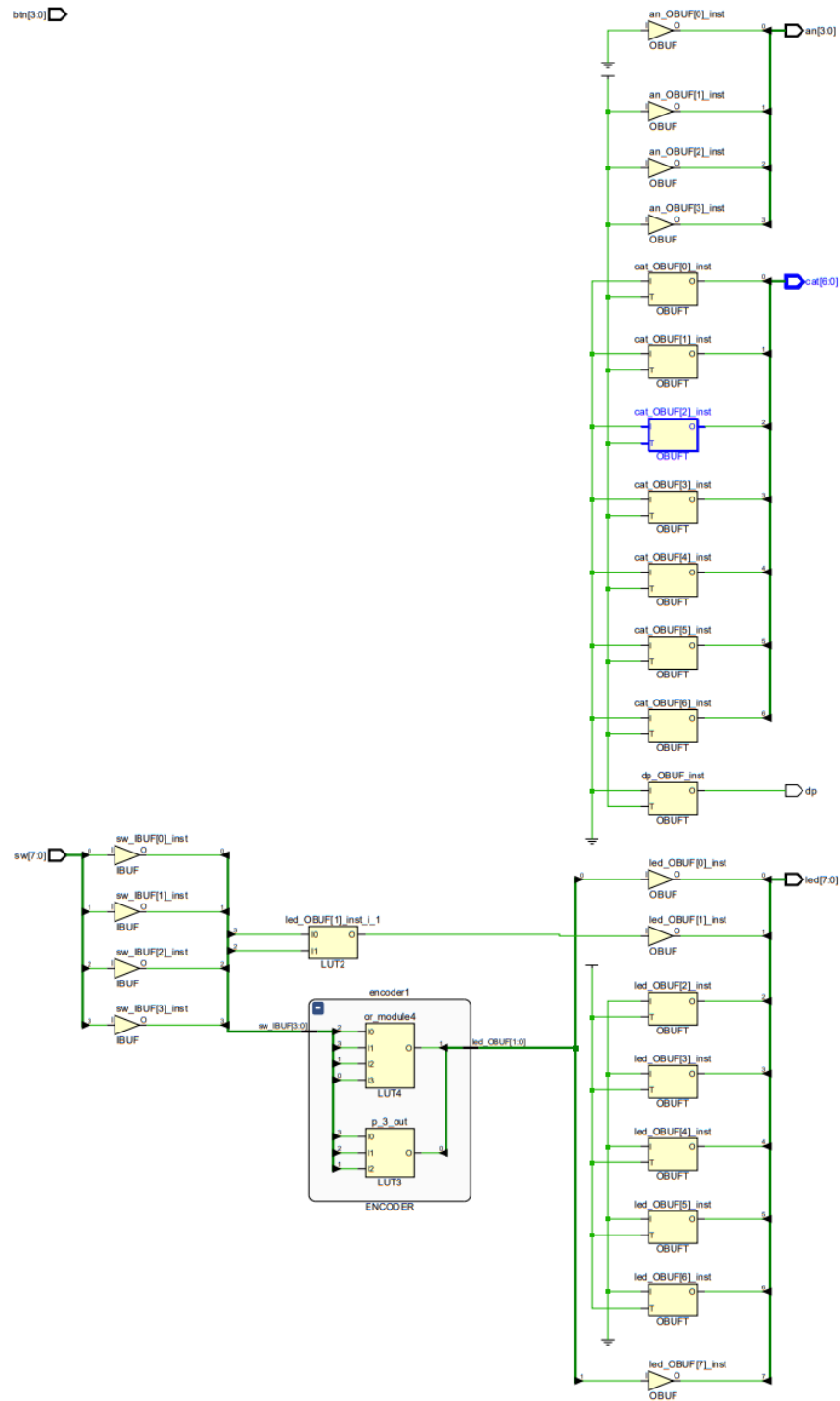


Figure 14: Priority Encoder Technology Schematic

## 2.6 Implementation Parts and Reports

The Timing report window displays a table of combinational delays. The left sidebar shows a tree view with 'Combinational Delays' selected. The table lists paths from input ports (sw) to output LEDs (led) with their respective maximum delays, process corners, and minimum delays.

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
sw[3]	led[7]	9.681	SLOW	3.091	FAST
sw[0]	led[7]	9.678	SLOW	3.011	FAST
sw[2]	led[7]	9.521	SLOW	2.960	FAST
sw[1]	led[7]	9.490	SLOW	2.915	FAST
sw[3]	led[0]	9.031	SLOW	2.801	FAST
sw[2]	led[0]	8.839	SLOW	2.675	FAST
sw[1]	led[0]	8.806	SLOW	2.628	FAST
sw[3]	led[1]	8.667	SLOW	2.642	FAST
sw[2]	led[1]	8.464	SLOW	2.504	FAST

Figure 15: Priority Encoder with Primitive Gates Implementation Part Report Timing Max Combinational Delay

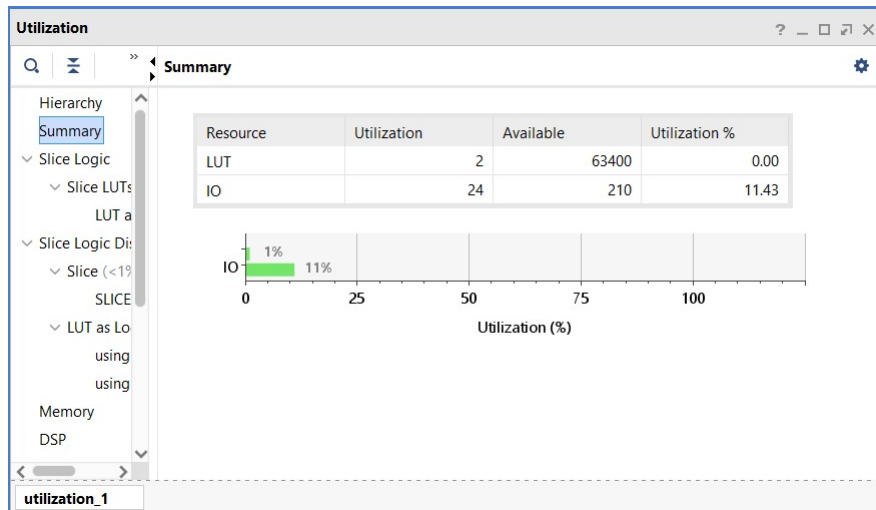


Figure 16: Priority Encoder with Primitive Gates Implementation Part Utilization Report

## 2.7 Behavioral Priority Encoder

Listing 7: Priority Encoder Behavioral Verilog Code

```

13 output reg [1:0] OUT,
14 output reg V );
15 always @(IN)
16     begin

```



```

17         casex (IN)
18             4'b0000:
19                 begin
20                     OUT = 2'bxx; V=0; end
21             4'b0001:
22                 begin
23                     OUT = 2'b00; V=1; end
24             4'b001x:
25                 begin
26                     OUT = 2'b01; V=1; end
27             4'b01xx:
28                 begin
29                     OUT = 2'b10; V=1; end
30             4'b1xxx:
31                 begin
32                     OUT = 2'b11; V=1; end
33         endcase
34     end
35 endmodule

```

## 2.8 Implementation Parts and Comparison Reports

Timing						
Combinational Delays						
From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner	
sw[3]	led[7]	9.330	SLOW	2.959	FAST	
sw[0]	led[7]	9.293	SLOW	2.885	FAST	
sw[3]	led[0]	9.256	SLOW	2.872	FAST	
sw[2]	led[7]	9.127	SLOW	2.822	FAST	
sw[1]	led[7]	9.105	SLOW	2.785	FAST	
sw[2]	led[0]	9.097	SLOW	2.740	FAST	
sw[1]	led[0]	9.049	SLOW	2.703	FAST	
sw[3]	led[1]	8.654	SLOW	2.650	FAST	
sw[2]	led[1]	8.463	SLOW	2.524	FAST	

Figure 17: Behavioral Priority Encoder Implementation Part Report Timing Max Combinational Delay

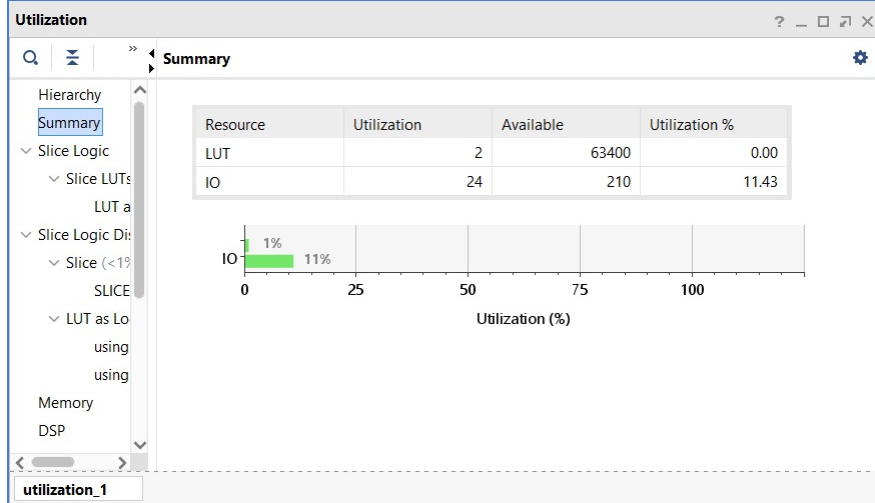


Figure 18: Behavioral Priority Encoder Implementation Part Utilization Report

When we compared the behavioral and structured design approaches, I observed that the behavioral design had a lower latency for various reasons, although there was no change in the functioning of the system used.

Behavioral design offers a higher-level approach when defining the functionality of a system. This allows for a clearer determination of what the system is supposed to do early in the design process.

Structural design is used to express more complex structures, but can be more difficult to optimize. This approach emphasizes the physical arrangement of components. It allows design errors to be detected earlier and helps in faster prototyping. In light of this information, it is natural that the behavioral design results in a lower delay, as we expected. To express it numerically, while the structural design delay time was 9.681, a decrease was observed by reducing the behavioral design delay time to 9.330.

Then, I made the module testable on FPGA by creating a bitstream.

### 3 MULTIPLEXER

I applied many steps in MUX in the same order as in Priority Encoder. Here, I coded the Multiplexer module twice - once for dataflow and once for behavioral. I added the MULTIPLEXER module I created to top\_module as multiplexer1, and provided the necessary input outputs as requested. In order to test the module I created, I wrote and simulated a testbench in which I tried appropriate cases. I observed RTL and Technology schematics. Afterwards, I created synthesis, implementation and bitstream in the same way. During the implementation phase, I commented the outputs of both codes below.

#### 3.1 Verilog Code, Testbench Code and Behavioral Simulation

Listing 8: MUX Verilog Code

```

1    input [1:0] S,
2    output 0
3);
4    wire temp1;
5    wire temp2;
6    wire temp3;
7    wire temp4;
8    assign temp1 = ~S[1] & ~S[0] & D[0];
9    assign temp2 = ~S[1] & S[0] & D[1];
10   assign temp3 = S[1] & ~S[0] & D[2];
11   assign temp4 = S[1] & S[0] & D[3];
12   assign 0 = temp1 | temp2 | temp3 | temp4 ;
13 endmodule

```

Listing 9: MUX Top\_Module Verilog Code

```

21    input [3:0] btn,
22    output [7:0] led,
23    output [6:0] cat,
24    output [3:0] an,
25    output dp);
26    MULTIPLEXER mux1(.D(sw[3:0]),.S(btn[1:0]),.O(led[0]));
27    assign an = 4'b1110;
28 endmodule

```

Listing 10: MUX Testbench Verilog Code

```

46    reg [3:0] BTN;
47    wire [7:0] LED;
48    wire [6:0] CAT;
49    wire [3:0] AN;
50    wire DP;
51    top_module uut(.sw(SW),.btn(BTN),
52                  .led(LED),.cat(CAT),.an(AN),.dp(DP));
53    initial
54    begin
55        BTN=2'b00; SW=4'b0001;
56        #10 BTN=2'b01; SW=4'b0010;
57        #10 BTN=2'b10; SW=4'b0100;
58        #10 BTN=2'b11; SW=4'b1000;
59        #10
60        $finish;
61    end
endmodule

```

What we observed in the simulation with the test bench we wrote to mux is; Depending on the value of the button, whatever value is in that index of the switch is observed on LED[0]. For example, when Btn is 00, sw[0], when Btn is 01, sw[1] button is 10, sw[2] button is 3, current values of sw[3] are displayed on LED [0].



Figure 19: Mux Behavioral Simulation

### 3.2 Rtl and Technology Schematic

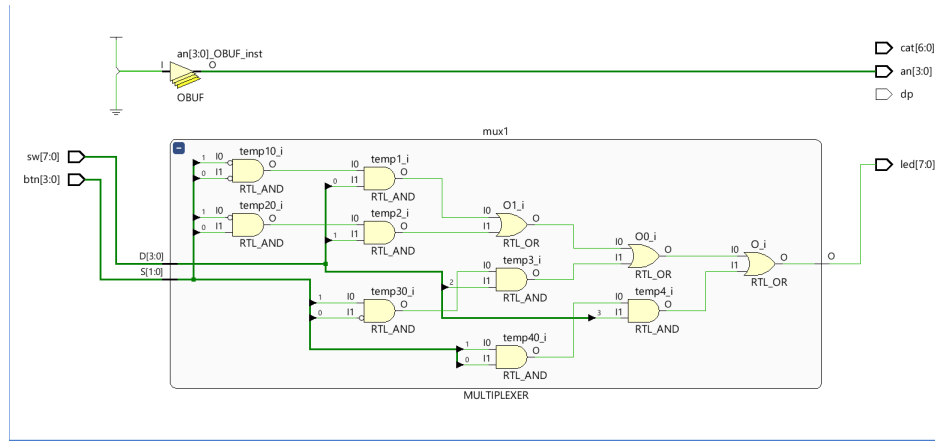


Figure 20: Mux Rtl Schematic

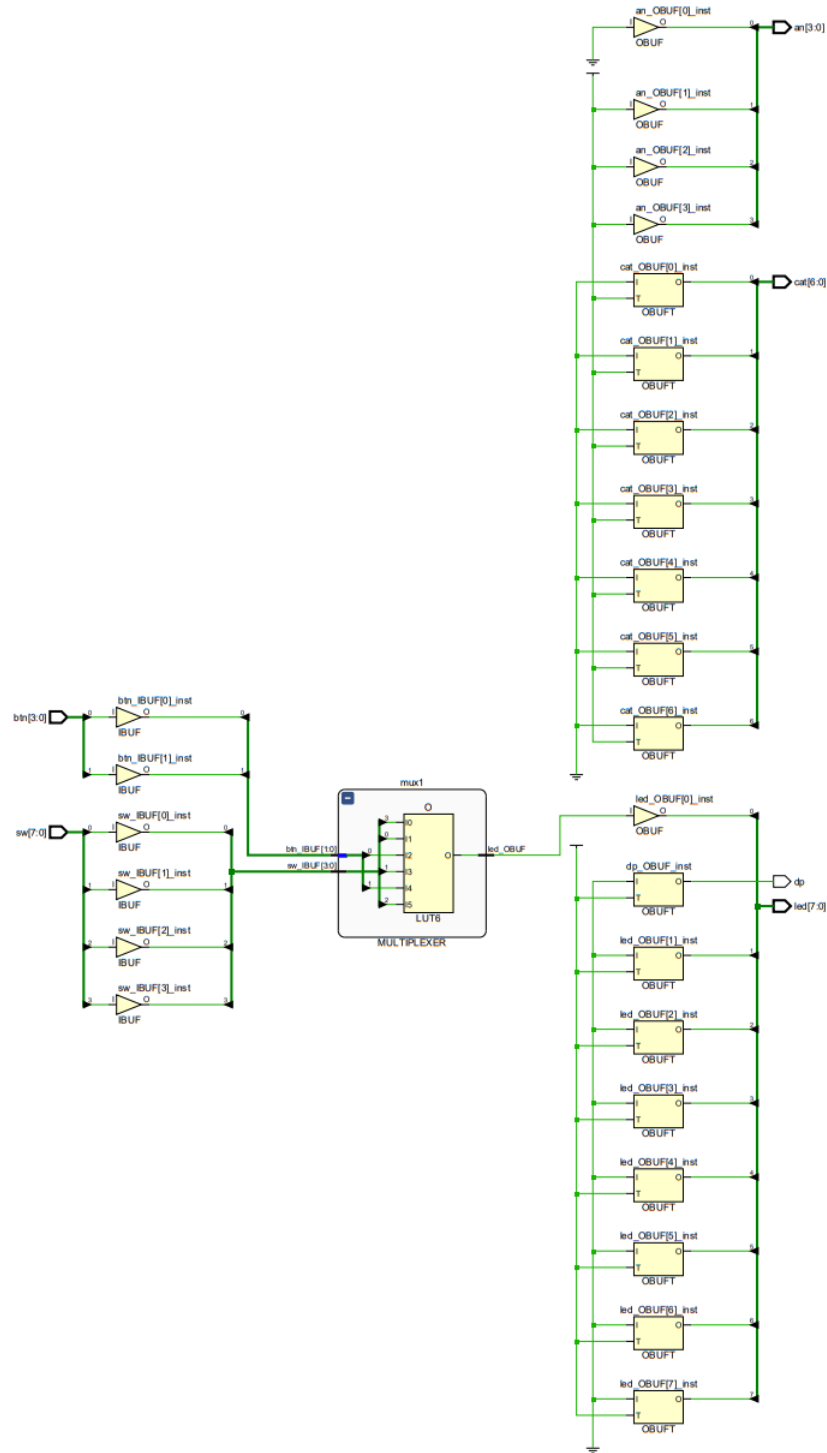


Figure 21: Mux Dataflow Code Technology Schematic



### 3.3 Implementation Parts and Reports

From Port	To Port	Max Delay	Max Process Corner	Min Delay	Min Process Corner
sw[3]	led[0]	9.241	SLOW	2.852	FAST
btn[0]	led[0]	9.167	SLOW	2.787	FAST
sw[0]	led[0]	8.980	SLOW	2.732	FAST
sw[1]	led[0]	8.944	SLOW	2.678	FAST
sw[2]	led[0]	8.634	SLOW	2.613	FAST
btn[1]	led[0]	8.411	SLOW	2.513	FAST

Figure 23: Mux Dataflow Code Implementation Part Report Timing Max Combinational Delay

 


Figure 24: Mux Dataflow Code Implementation Part Utilization Report

### 3.4 Behavioral MULTIPLEXER

Listing 11: MUX Behavioral Verilog Code

```

14     input [1:0] S,
15     output reg O
16 );
17 always @(*)
18 begin
19     case (S)
20         2'b00: O = D[0];
21         2'b01: O = D[1];
22         2'b10: O = D[2];
23         2'b11: O = D[3];
24         default: O = 1'b0;
25     endcase
26 end
27 endmodule

```

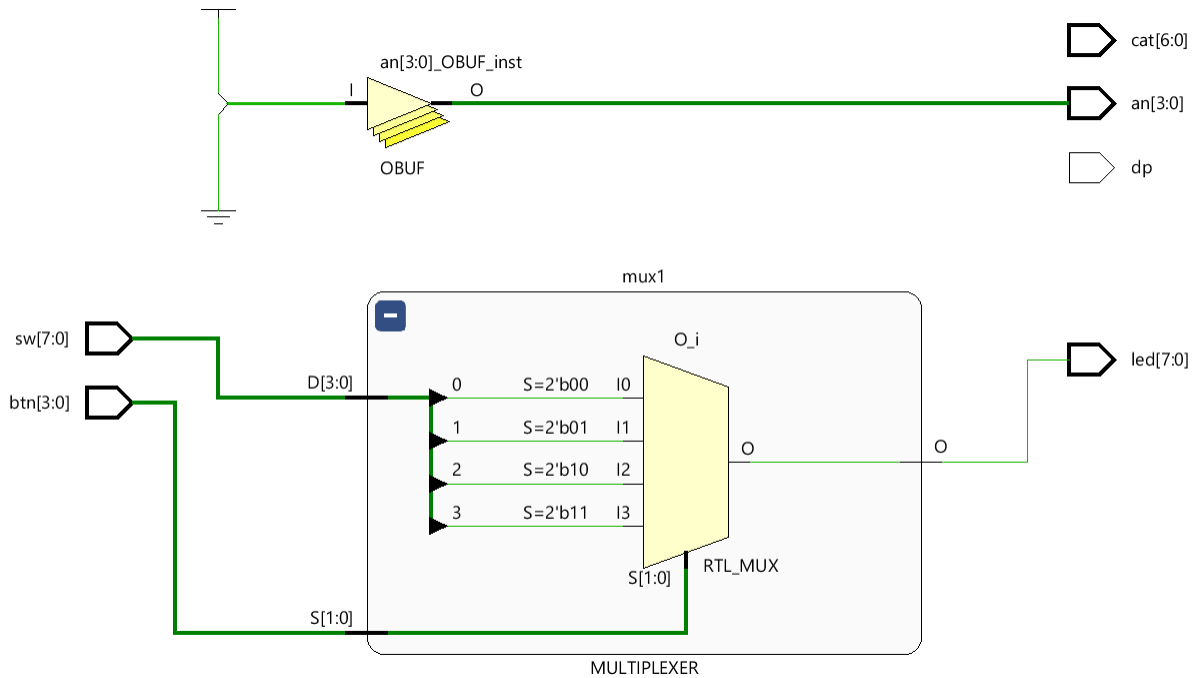


Figure 25: Mux Behavioral Code Rtl Schematic

### 3.5 Implementation Parts and Comparison Reports

Both reports came out the same: max combinational delay is 9.241 with sw[3] to led[0] where 1 lut using. We do not observe the timing difference here that we observe in the encoder. Although directly giving the result in the behavioral simulation can save time in many cases, there does not appear to be any delay in timing since there are not many logic gates here. In both cases, max\_delay was observed to be 9.241 sw[3]to led[0].

Then, I made the module testable on FPGA by creating a bitstream.

## 4 DEMUX

### 4.1 Verilog Code, Testbench Code and Behavioral Simulation

To create the demux module as requested, I created a structural module using the AND, NOT, TRI gates in the SSI\_Library which I created last week. I set top\_module according to Demux as it says in the report. I created the testbench by valuing the inputs in order to observe all states of the DEMUX structure.

Listing 12: Demux Verilog Code

```

62     output [3:0] 0
63 );
64 wire temp1;
65 wire temp2;
```



```

66 NOT not_S0( .O(temp1),.I(S[0]));
67 NOT not_S1(.O(temp2), .I(S[1]));
68
69 wire temp3;
70 AND and_NS1NS0(.O(temp3), .I1(temp2),.I2(temp1));
71 TRI tri_module00(.O(O[0]), .I(D), .E(temp3));
72
73 wire temp4;
74 AND and_NS1S0(.O(temp4), .I1(temp2),.I2(S[0]));
75 TRI tri_module01(.O(O[1]), .I(D), .E(temp4));
76
77 wire temp5;
78 AND and_S1NS0(.O(temp5), .I1(S[1]),.I2(temp1));
79 TRI tri_module02(.O(O[2]), .I(D), .E(temp5));
80
81 wire temp6;
82 AND and_S1S0(.O(temp6), .I1(S[1]),.I2(S[0]));
83 TRI tri_module03(.O(O[3]), .I(D), .E(temp6));
84
85 endmodule

```

Listing 13: Top\_Module Demux Verilog Code

```

29 input [3:0] btn,
30 output [7:0] led,
31 output [6:0] cat,
32 output [3:0] an,
33 output dp);
34
35 DEMULTIPLEXER demux1(.D(sw[0]),.S(btn[1:0]), .O(led[3:0]));
36 assign an = 4'b1110;
37 endmodule

```

Listing 14: Demux Testbench Verilog Code

```

86 reg [3:0] BTN;
87 wire [7:0] LED;
88 wire [6:0] CAT;
89 wire [3:0] AN;
90 wire DP;
91 top_module uut(.sw(SW),.btn(BTN),
92               .led(LED),.cat(CAT),.an(AN),.dp(DP));
93 initial
94     begin
95         SW[0]=1; BTN=2'b00;
96         #10 BTN=2'b01;

```

```

96         #10 BTN=2'b10;
97         #10 BTN=2'b11;
98         #10
99         $finish;
100     end
101 endmodule

```

What we observed on Demux's test bench; According to the value of the two-bit buttons, the index of the LED at that value (if the button is 11, it is led[3], if the button is 00, it is led [0], if the button is 01, it is led [1, if it is button10, it is led[2]), whichever value the switch is on at that moment. Here, we have observed that our module is correct by giving 0 and 1 values to the switches.



## 4.2 Rtl and Technology Schematic

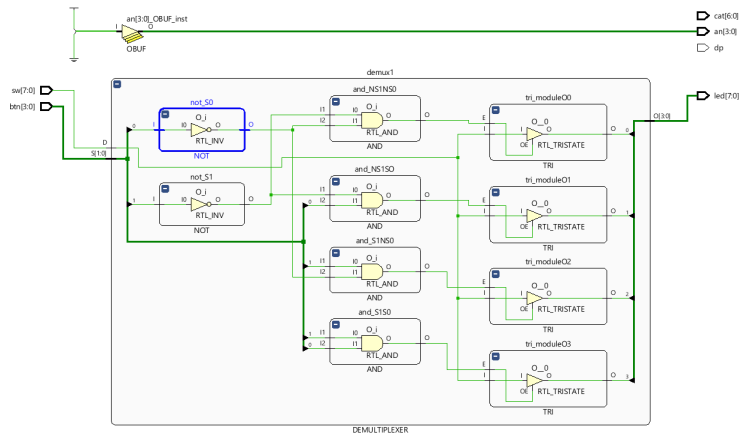


Figure 27: Demux Rtl Schematic

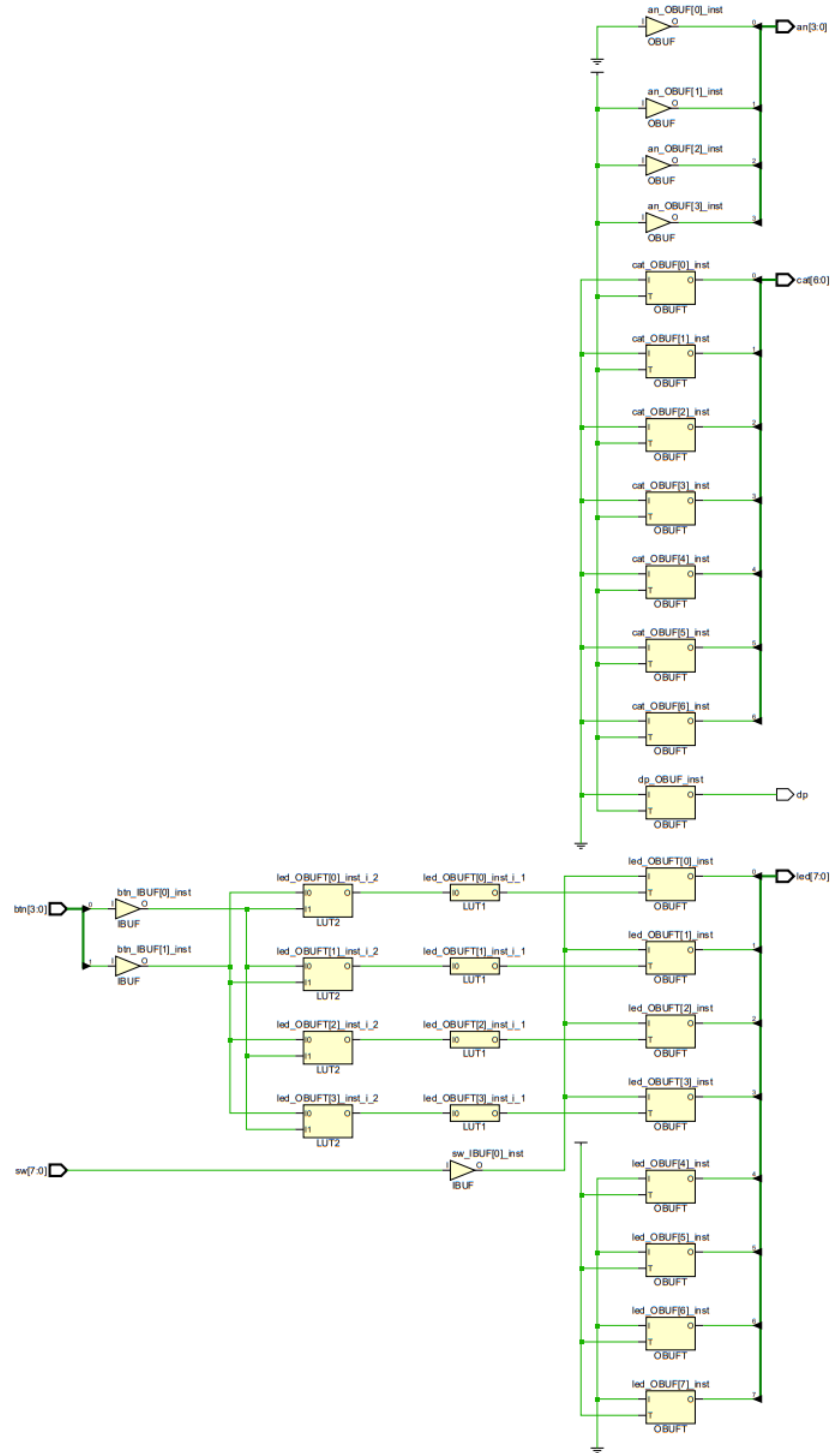


Figure 28: Demux Technology Schematic

### 4.3 Implementation Parts and Reports

Combinational Delays						
From Port	To Port	M a	Max Process Corner	Min Delay	Min Process Corner	
btn[1]	led[0]	9.004	SLOW	2.575	FAST	
btn[0]	led[0]	8.941	SLOW	2.594	FAST	
btn[1]	led[3]	8.699	SLOW	2.423	FAST	
btn[1]	led[2]	8.681	SLOW	2.454	FAST	
btn[0]	led[2]	8.662	SLOW	2.479	FAST	
btn[0]	led[3]	8.647	SLOW	2.454	FAST	
btn[1]	led[1]	8.294	SLOW	2.299	FAST	
btn[0]	led[1]	8.263	SLOW	2.312	FAST	
sw[0]	led[3]	7.600	SLOW	2.144	FAST	
sw[0]	led[2]	7.529	SLOW	2.118	FAST	
sw[0]	led[0]	7.356	SLOW	2.031	FAST	
sw[0]	led[1]	6.971	SLOW	1.872	FAST	

Figure 29: Demux Report Timing Summary Combinational Delays

 


Figure 30: Demux Utilization Summary

Then, I made the module testable on FPGA by creating a bitstream.